

Hulme's Circuit Practice 2 – determine all unknown currents & the voltages across each resistor.



